

Device Information

ISL986035 Channel DC/DC Converter + V_{ON} Slice + Power-Good[Print Page](#)

- [Features Description](#)
- [Technical Documentation](#)
- [Pricing / Samples](#)
- [iSim Design Simulation](#)
- [Tools And Support](#)
- [Related Devices](#)

Datasheet**ISL98603**5 Channel DC/DC Converter + V_{ON} Slice + Power-Good

Input Voltage (V)	9.5 to 15
V _{BOOST} (V)	10.83 to 19
Boost Current Limit (A)	5
V _{ON} (V)	up to 36
V _{OFF} (V)	down to -10
V _{LOGIC} (V)	(V _{logic1}) 2.5 to 3.3 (V _{logic2}) 0.9 to 2.0
# of V _{COM}	N/A
# of Gamma	N/A
Features	Automatic Start-Up Sequencing, fault protection
Input Voltage (min) (V)	9.5
Input Voltage (max) (V)	15
V _{BOOST} (min) (V)	10.83
V _{BOOST} (max) (V)	19
V _{ON} (max) (V)	36
V _{OFF} (min) (V)	-10
V _{LOGIC} (min) (V)	2.5, 0.9
V _{LOGIC} (max) (V)	3.3, 2

Product Information**Key Features**

- 9.5V to 15.0V Input Supply
- 1.3MHz Switching Frequency
- 5.0A Integrated Boost for Up to 19V A_{VDD}
- V_{ON} Charge Pump, Up to 36V and 120mA
- V_{OFF} Charge Pump, Down to -10V and 120mA
- Synchronous Buck1 for 3.3V/2.5V with 2.0A Peak FET
- Synchronous Buck2 Controller Output from 0.9V to 2.0V
- A_{VDD} Delay Switch Capable of Soft-starting into a Highly Capacitive, Heavy Load
- V_{ON} Slice Function Integrated
- Power-Good Function for TCON Enable
- Automatic Start-Up Sequencing
- UVLO, UVP, OVP, OCP, and OTP Protection
- 40 Ld 6x6 QFN
- Specified for Ambient Operation Over the -40°C to +85°C Temperature Range
- Pb- Free (RoHS Compliant)

Description

The ISL98603 represents a high power, integrated LCD supply IC targeted at large panel LCD displays. The ISL98603 integrates a high power boost converter for A_{VDD} generation, V_{ON} and V_{OFF} charge pump drivers, one synchronous buck regulator, and one synchronous buck controller for 2 logic voltages. The V_{ON} slicing circuitry and power-good function are also included.

Operating at 1.3MHz, the A_{VDD} boost converter features a 5.0A boost FET. Feedback is taken from the far side of the delay FET for improving regulation. The OVP circuit protects output side components.

The logic synchronous buck converter features two 2.3A FETs operating at 1.3MHz internal clock. The output voltage is set by the IC internally or feedback resistor. The soft-start circuitry are also integrated with the buck.

The second logic voltage is generated from synchronous buck converter with MOSFET controllers. The overcurrent protection is also integrated with the buck.

The charge pump of V_{ON} and V_{OFF} use the full switching frequency and integrates the driver for high current capability. V_{ON} is further processed through an integrated V_{ON} Slice circuit in order to reduce flicker.

Alternative fixed voltages at the boost, Buck1, Buck2, V_{ON} charge pump, and V_{OFF} charge pump are available in ISL98603, please contact Intersil Marketing via email at rmonteir@intersil.com.

Packaging / Samples / Ordering



iBuy direct from Intersil



iBuy direct - out of stock



Request samples



Check distributor inventory



Available in RoHS/Pb-Free

Part No.	Design-In Status	Temp.	Package	MSL	Pb		
ISL98603IRAAZ	Active	Ind	40 Ld QFN	3	✓		
ISL98603IRAAZ-T	Active	Ind	40 Ld QFN T+R	3	✓		
ISL98603IRAAZ-T7A	Active	Ind	40 Ld QFN T+R	3	✓		
ISL98603IRAAZ-TK	Active	Ind	40 Ld QFN T+R	3	✓		

MSL = Moisture Sensitivity Level - per IPC/JEDEC J-STD-020

SMD = Standard Microcircuit Drawing

Technical Documentation

Datasheet(s):

[EN](#) 5 Channel DC/DC Converter + V_{ON} Slice + Power-Good

Technical Homepage:

[Display Products](#)

Tools And Support

iSim Design Simulation

No Models Available

Applications

LCD TV



Related Devices



Parametric Table

EL7515	High Frequency PWM Step-Up Regulator
EL7520	4-Channel DC/DC Controller
EL7520A	4-Channel DC/DC Controller
EL7581	3-Channel DC/DC Converter
EL7583	3-Channel DC/DC Converter
EL7586	TFT-LCD Power Supply
EL7586A	TFT-LCD Power Supply
EL7640	TFT-LCD DC/DC with Integrated Amplifiers

EL7640A	TFT-LCD DC/DC with Integrated Amplifiers
EL7641	TFT-LCD DC/DC with Integrated Amplifiers
EL7641A	TFT-LCD DC/DC with Integrated Amplifiers
EL7642	TFT-LCD DC/DC with Integrated Amplifiers
EL7642A	TFT-LCD DC/DC with Integrated Amplifiers
ISL78010	Automotive Grade TFT-LCD Power Supply
ISL78020	Automotive Grade TFT-LCD DC/DC with Integrated Amplifiers
ISL78022	Automotive Grade TFT-LCD DC/DC with Integrated Amplifiers
ISL97516	600kHz/1.2MHz PWM Step-Up Regulator
ISL97519	1% Output Accuracy 600kHz/1.2MHz PWM Step-Up Regulator
ISL97519A	600kHz/1.2MHz PWM Step-Up Regulator
ISL97522	4-Channel TFT-LCD Supply
ISL97536	Monolithic 1A Step-Down Regulator with Low Quiescent Current
ISL97642	TFT-LCD DC/DC with Integrated Amplifiers
ISL97645	Boost + V _{ON} Slice + V _{COM}
ISL97645A	Boost + V _{ON} Slice + V _{COM} + Reset
ISL97646	Boost + LDO + V _{ON} Slice + V _{COM}
ISL97650	4-Channel Integrated LCD Supply
ISL97650B	4-Channel Integrated LCD Supply
ISL97651	4-Channel Integrated LCD Supply
ISL97652	4-Channel Integrated LCD Supply with Dual V _{COM} Amplifiers
ISL97653A	5-Channel Integrated LCD Supply
ISL97656	640kHz/1.2MHz PWM Step-Up Regulator
ISL98012	1.8V Input PWM Step-Up Regulator
ISL98602	5 Channel DC/DC Converter + V _{ON} Slice + Power Good